Computer Architecture: Gates and Wires


Brent van Bladel Stephen Pauwels





Gates and Wires


- Introduction to CA from Boolean Theory
- Introduction to Logisim


U	
	Logisim: main of Untitled
👆 💺 A 🖻 🔍 ⊳ D D	
🖉 🏟 🔝 🖺	
+ + # ×	
🚞 Untitled	
onuted	
Q main ▶ ■ Wiring	
🕨 🚞 Gates	
Plexers	
Arithmetic	
🕨 🚞 Memory	
Input/Output	
🕨 🚞 Base	

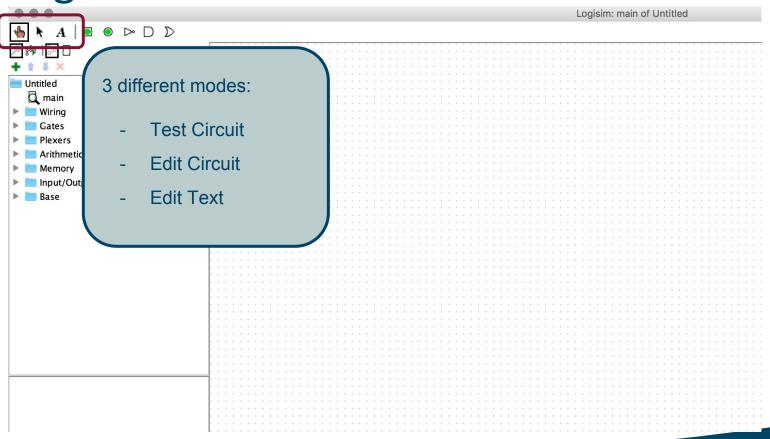


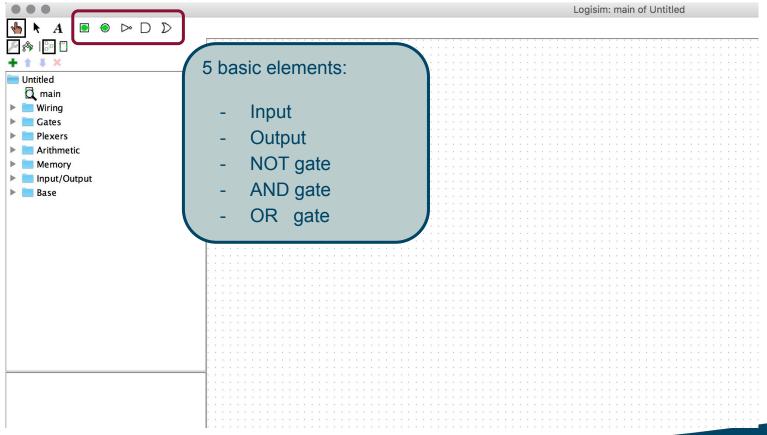


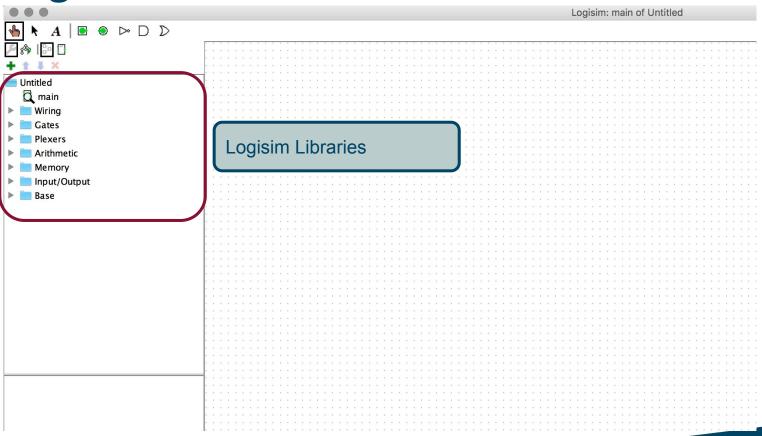


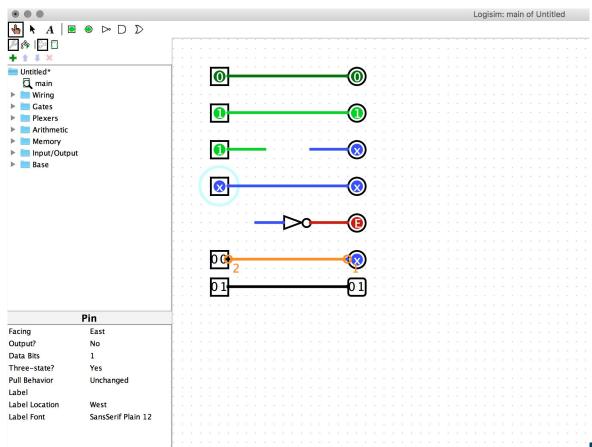


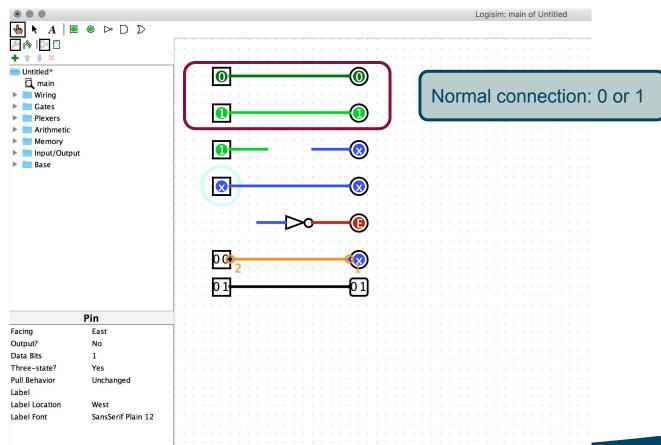

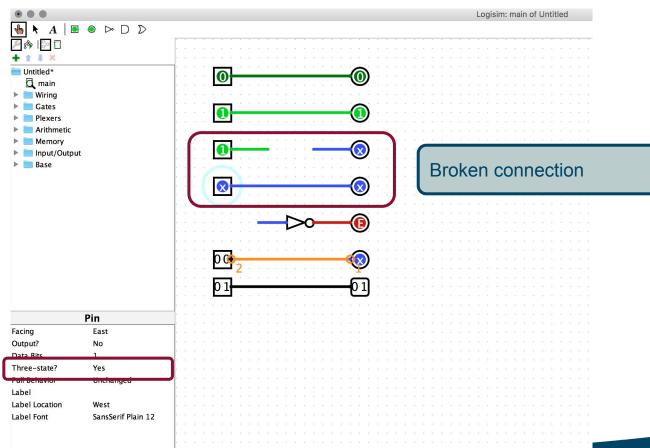

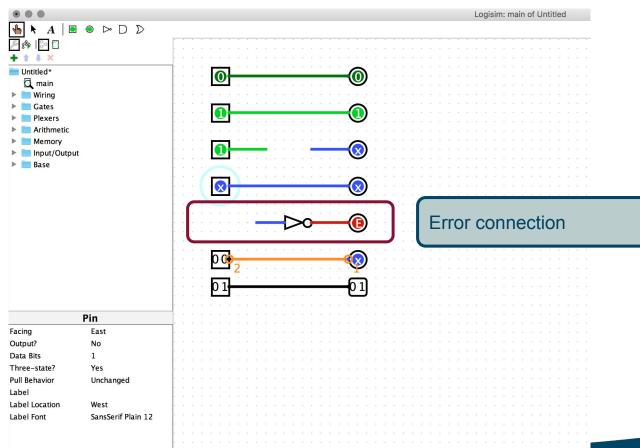

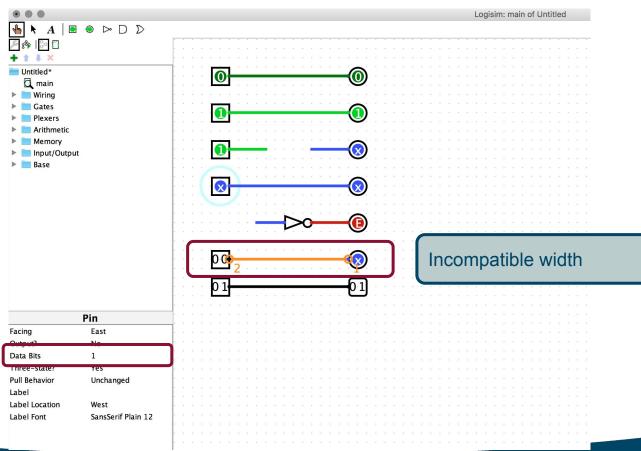

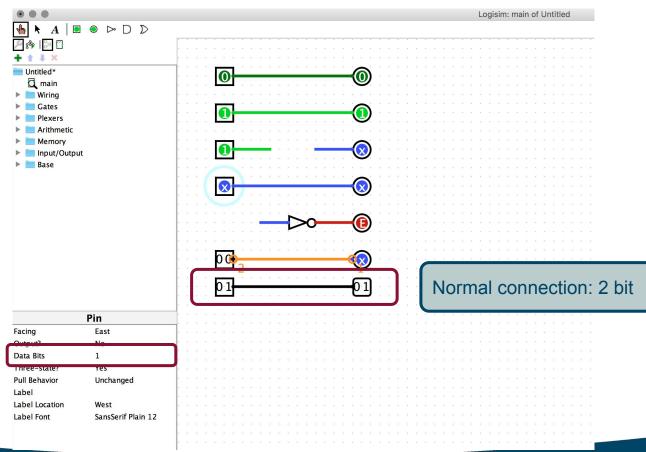


• • •		Logisim: test of Untitled
👆 📐 A 🖻 🔍 🗁 D Σ	>	
۵ 🗗 🎦		
+ t # X		
Untitled*		
🖸 main		
🛱 test		
Wiring		
Gates		
Plexers Arithmetic		
Arithmetic Memory		
Input/Output		
Base		
		a ta ta ta a lat ta a a at ta a a ta ta




• • •		Logisim: test of Untitled
👆 📐 A │ 🖻 🐵 D D		
Untitled*	ircuits to library	
🚺 main Q test		
Wiring		
Gates Plexers		
Arithmetic		
Memory Input/Output		
▶ 🛅 Base		



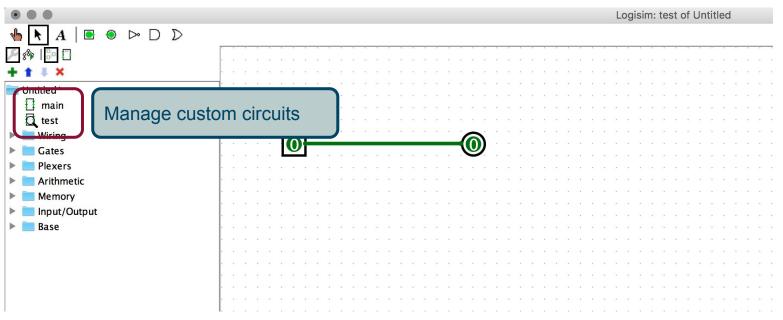



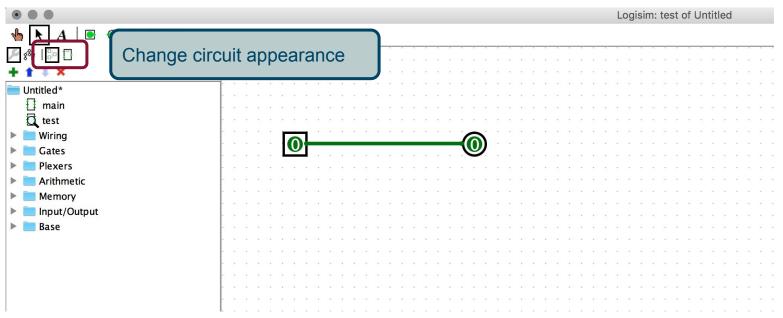



		Logisim: main of Untitled
A 🖻 🖲 🗁 D D		
🖚 🔝 🖸		
1 I X		
Untitled*		
a main		
🗓 test		
Wiring Wiring		
🔜 Gates		
Plexers		
Arithmetic		
Memory		
Input/Output		
Base		
	Use custor	n circuit in other circuits t
	introduce	photraction lovers
		abstraction layers.

